Lab-5: The BJT Biasing Circuit

Name: Raihan Ahammed ID: 2532600043 Group: 06

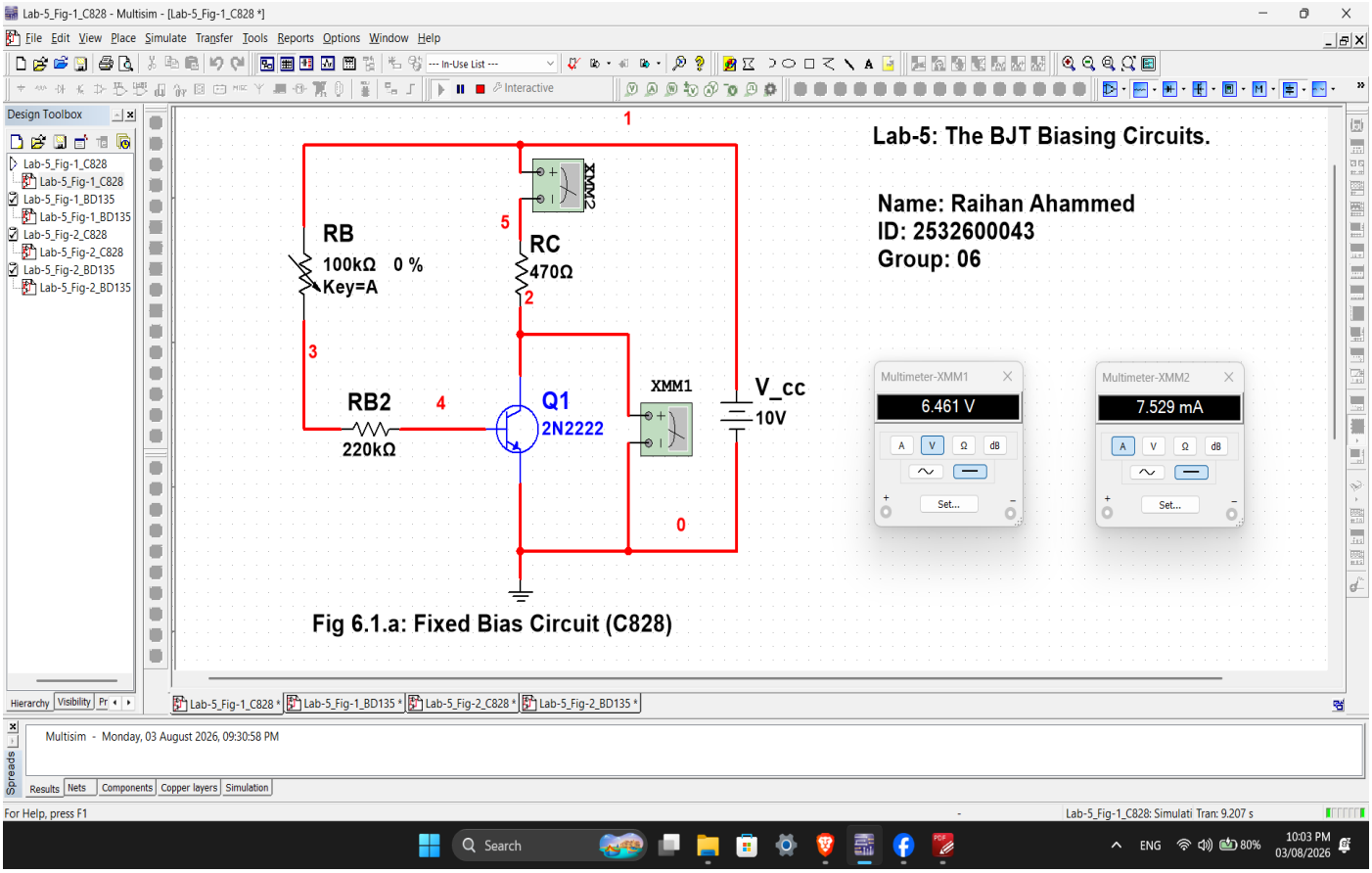


Fig 6.1.a: Fixed Bias Circuit (C828)

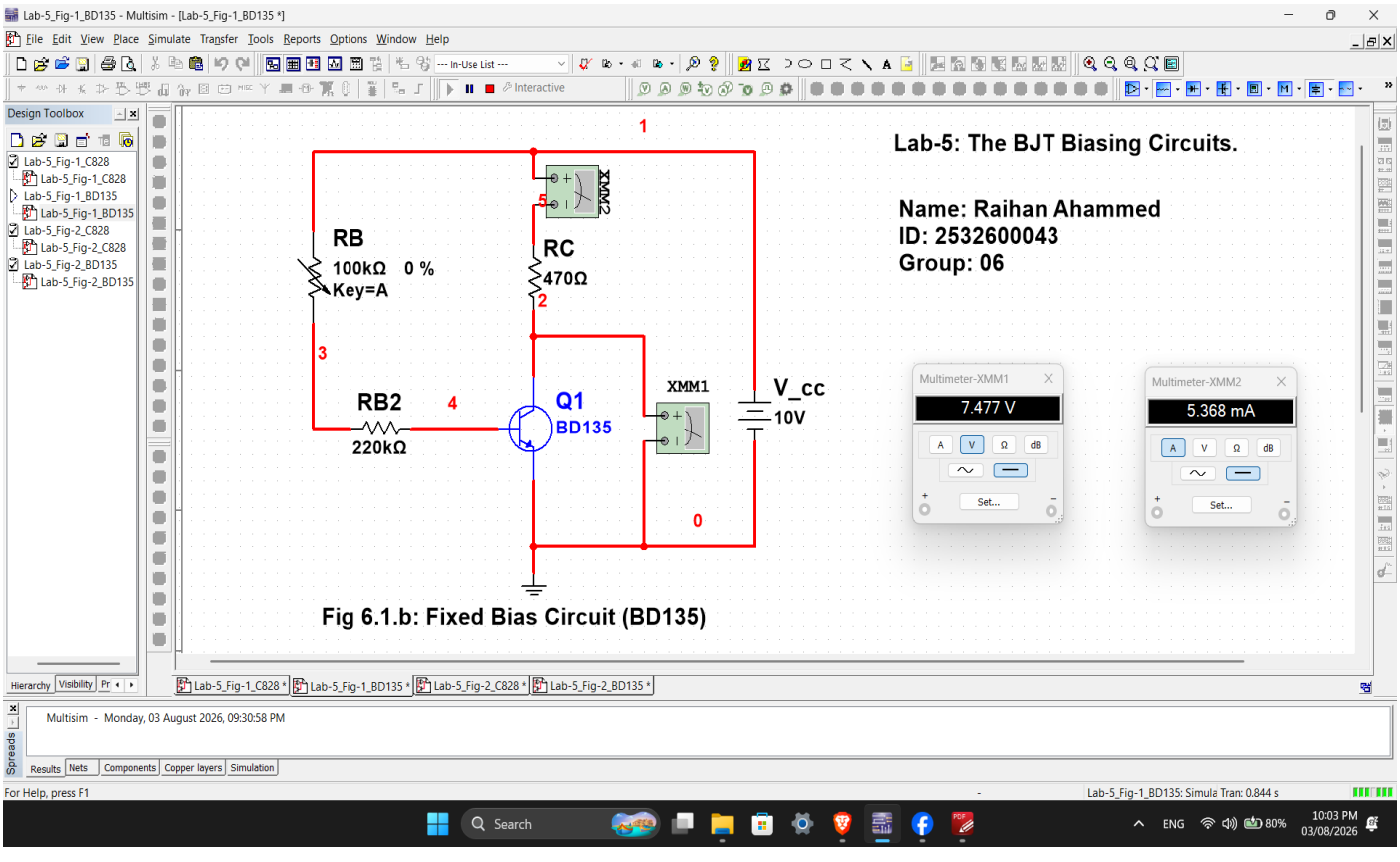


Fig 6.1.b: Fixed Bias Circuit (BD135)

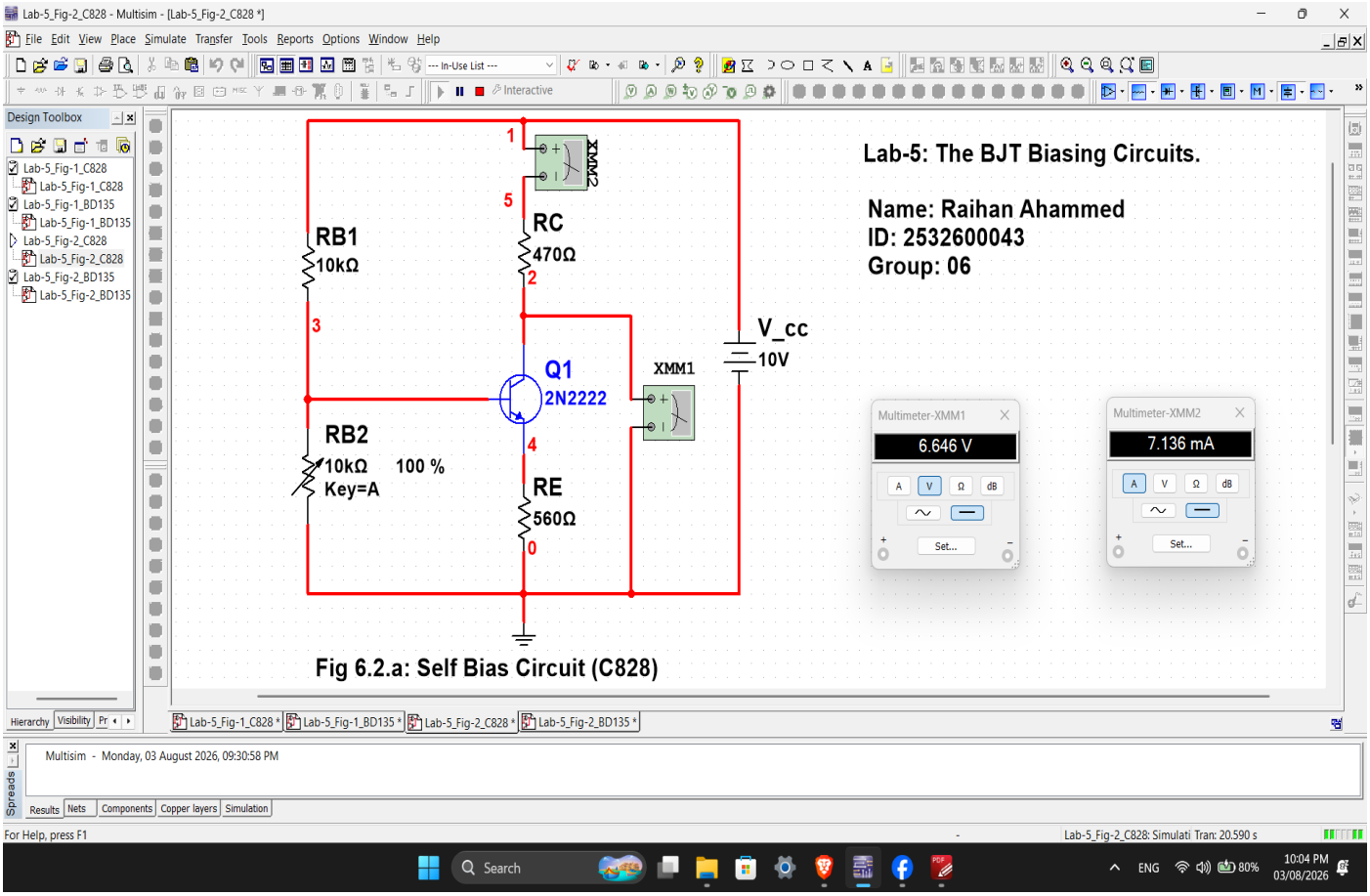


Fig 6.2.a: Self Bias Circuit (C828)

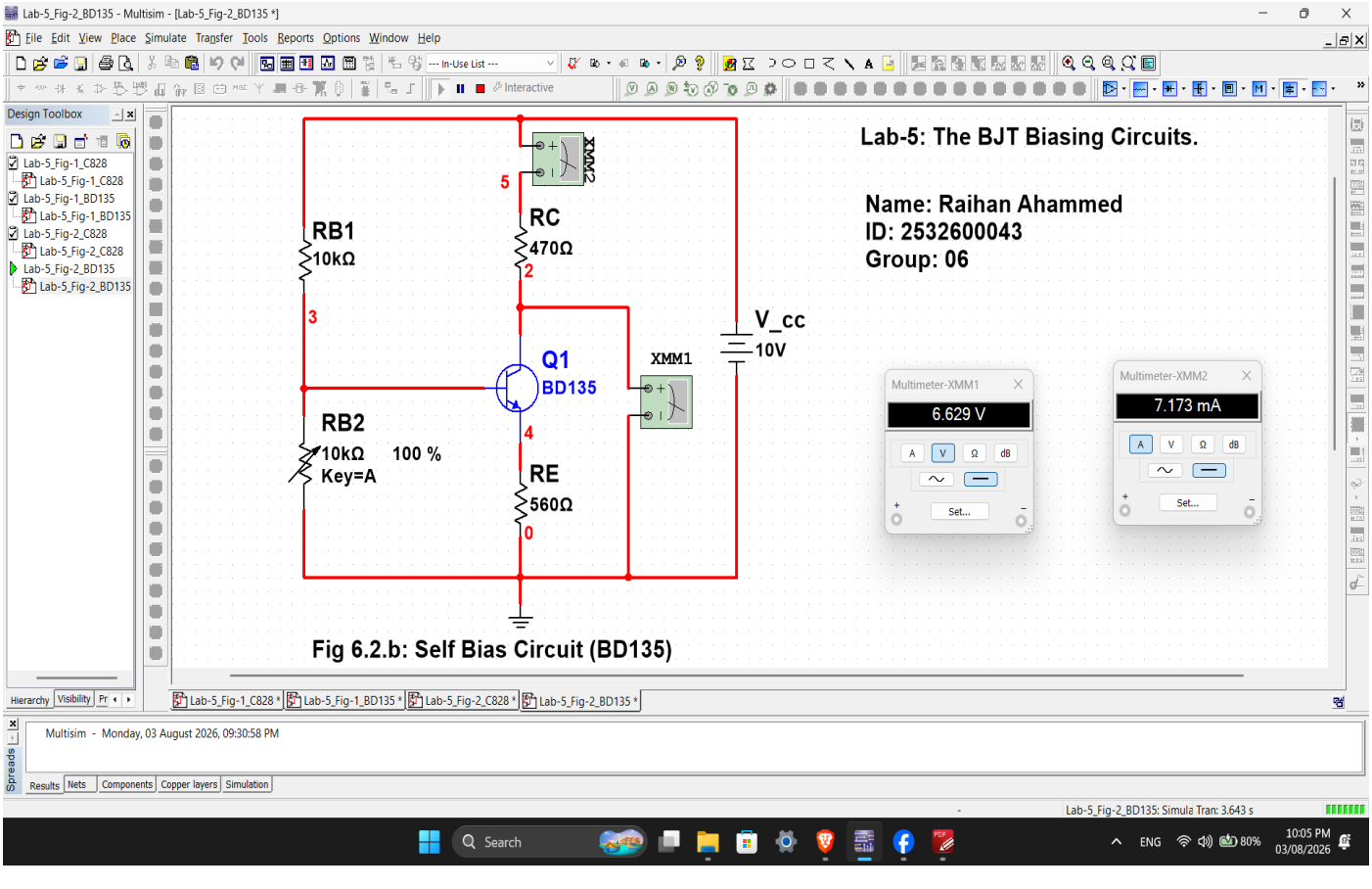


Fig 6.2.b: Self Bias Circuit (BD135)